

# Computer Organization (2024-Fall)

## Final Project - Simple Processor

### Design Description

A processor executes operations specified in the form of instructions. In this project, a string of instructions will be given. Your job is to decode these instructions and execute.

- The following is the basic required instruction format: (similar to MIPS)

Type	Fields (32 bits)					
R-type	opcode (6)	rs (5)	rt (5)	rd (5)	shamt (5)	funct (6)
I-type	opcode (6)	rs (5)	rt (5)	immediate (16)		
Jump	opcode (6)	address(26)				

Register s(rs), Register t(rt) and Register d(rd) represent the address of registers. Since the instruction takes 5 bits to store the address, it means we have 32 registers, from r[0] to r[31]. Each register reserve 32 bits to store data, e.g. rs = 5'b00000 means one of operands is "r[0]". rt = 5'b00101 means one of operands is "r[5]", and so on. The register file [31:0] r[0:31] have been declared by TA in SP.v. **DO NOT** edit the name of register file, or TA's pattern would catch wrong results.

- The following is the required instruction set of this design:

Type	Function	Description	opcode	funct
R-type	and	$R[\$rd] \leftarrow R[\$rs] \& R[\$rt]$	0x00	0x00
	or	$R[\$rd] \leftarrow R[\$rs] \mid R[\$rt]$	0x00	0x01
	add	$R[\$rd] \leftarrow R[\$rs] + R[\$rt]$	0x00	0x02
	sub	$R[\$rd] \leftarrow R[\$rs] - R[\$rt]$	0x00	0x03
	slt	if( $R[\$rs] < R[\$rt]$ ) $R[\$rd] \leftarrow 1$ else $R[\$rd] \leftarrow 0$	0x00	0x04
	sll	$R[\$rd] \leftarrow R[\$rs] \ll \text{shamt}$	0x00	0x05
	nor	$R[\$rd] \leftarrow \sim(R[\$rs] \mid R[\$rt])$	0x00	0x06
	jr	$PC \leftarrow R[\$rs]$	0x00	0x07
I-type	andi	$R[\$rt] \leftarrow R[\$rs] \& \text{ZE}(\text{imm})$	0x01	
	ori	$R[\$rt] \leftarrow R[\$rs] \mid \text{ZE}(\text{imm})$	0x02	
	addi	$R[\$rt] \leftarrow R[\$rs] + \text{SE}(\text{imm})$	0x03	

	subi	$R[\$rt] \leftarrow R[\$rs] - SE(imm)$	0x04	
	lw	$R[\$rt] \leftarrow Mem(R[\$rs] + SE(imm))$	0x05	
	sw	$Mem(R[\$rs] + SE(imm)) \leftarrow R[\$rt]$	0x06	
	beq	if( $R[\$rs] == R[\$rt]$ ) $PC \leftarrow PC + 4 + SE(\{imm, 00\})$	0x07	
	bne	if( $R[\$rs] != R[\$rt]$ ) $PC \leftarrow PC + 4 + SE(\{imm, 00\})$	0x08	
	lui	$R[\$rt] \leftarrow \{imm, 0x0000\}$	0x09	
Jump	j	$PC \leftarrow \{PC[31:28], address[25:0] \ll 2\}$	0x0a	
	jal	$R[31] \leftarrow PC + 4$ $PC \leftarrow \{PC[31:28], address[25:0] \ll 2\}$	0x0b	

In the above table, SE or ZE mean doing sign extension or zero extension on the number. There will be a  $4096 * 32$  data memory in this project. You can access this memory according to the instruction.

The pattern also be used as instruction memory in this project. You should access pattern with `inst_addr` (PC) to get next instruction. Be careful of the 4 bytes offset.

## Design Inputs and Outputs

- The following are the definitions of input signals.

Input Signal	Connection	Bit Width	Description
clk	PATTERN	1	Positive edge trigger clock.
rst_n	PATTERN	1	Asynchronous active-low reset.
in_valid	PATTERN	1	High when <b>inst</b> is valid.
inst	PATTERN	32	Instruction given be pattern.
mem_dout	MEM	32	Data output from memory according to <b>mem_addr</b> .

- The following are the definitions of output signals.

Output Signal	Connection	Bit Width	Description
out_valid	PATTERN	1	Pattern will give next Instruction according to <b>inst_addr</b> if <b>out_valid</b> is high.
inst_addr	PATTERN	32	Next instruction address. (PC)
mem_wen	MEM	1	When <b>WEN</b> is high, you can load data from memory. When <b>WEN</b> is low, you can write data into memory.
mem_addr	MEM	12	Data memory address input.

mem_din	MEM	32	Data memory data input
---------	-----	----	------------------------


## Specification

1. Top module name: SP (Design file name: SP.v)
2. It is **asynchronous** and **active-low reset**. If you use synchronous reset in your design, you may fail to reset signals.
3. The reset signal (**rst\_n**) would be given only once at the beginning of simulation.
4. **inst\_addr**, **out\_valid** and **register file r** should be reset after the reset signal is asserted.
5. The **out\_valid** is limited to be high for only **1 cycle** in non-pipeline design.
6. **out\_valid** should not be raised when **in\_valid** is high for non-pipeline design.
7. The **out\_valid** should be raised within 10 cycles after **in\_valid** raised.
8. Next instruction will be given in the next cycle after **out\_valid** is raised.
9. Pattern will check the **register file r result** and **inst\_addr** for each instruction at clock negative edge when **out\_valid** is high.
10. Pattern will check the final result of mem.v.
11. Released and demo pattern will not cause overflow.

## Additional specification for pipelined design


12. Use the same **instruction.txt** and **mem.txt** file as non-pipeline design.
13. Use **TESTBED.v**, **PATTERN.v** to test **non-pipeline** design.
14. Use **TESTBED\_p.v**, **PATTERN\_p.v** to test **pipeline** design.
15. No need to consider branch prediction. The correct **inst\_addr** should be given by design after **beq/bne** instructions fetched.
16. No need to consider data hazards. data dependency or load-use will be separated by at least two instructions to avoid data hazards in pattern.
17. Once **out\_valid** raised, it should be kept high until simulation end.
18. Pattern will check the sequence **inst\_addr**.

## Block Diagram

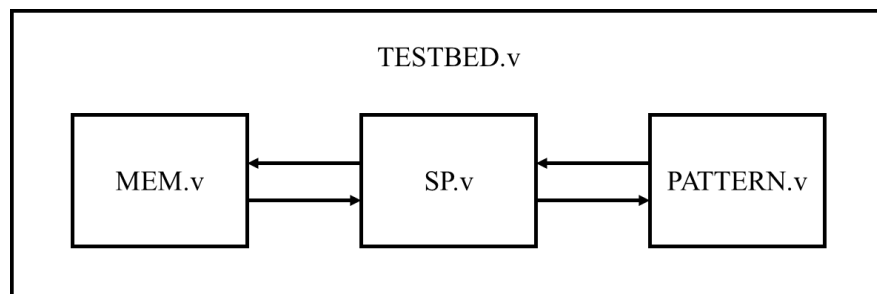


## Example Waveform

### Non-pipeline

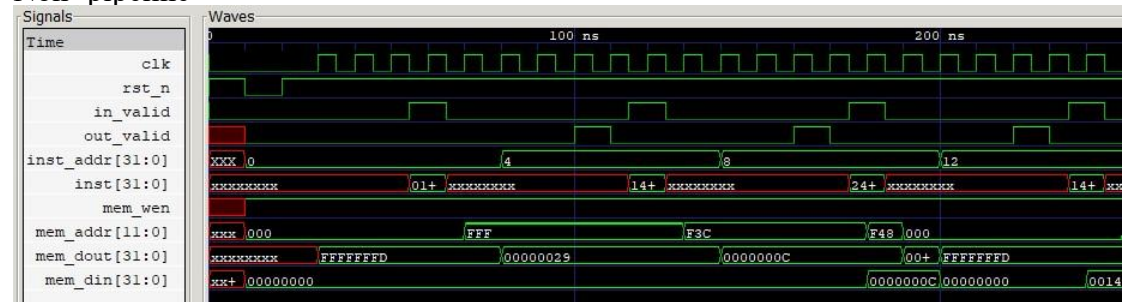

### Pipeline

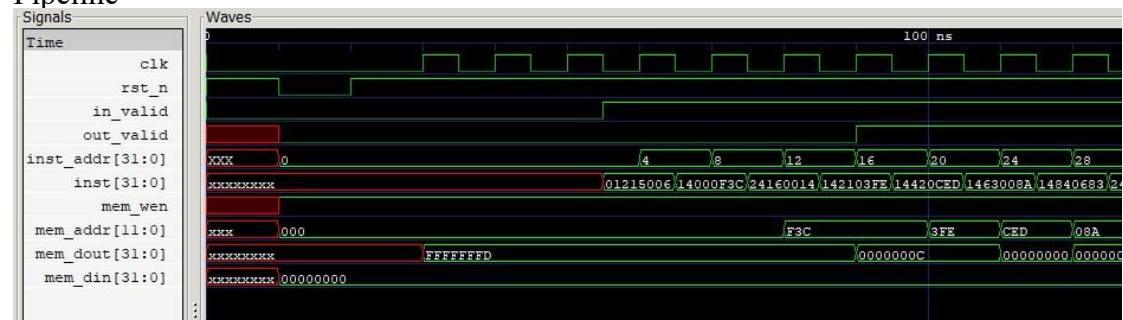

## Grading Policy

- Generate your PATTERN.v/PATTERN\_p.v & Pass TA's design: 30%
- Non-pipelined design (SP.v) pass TA's pattern: 30%
- Pipelined design (SP\_pipeline.v) pass TA's pattern: 40%
- Bonus: Show your project design methods in report. (1) Methods of generate pattern (2) Design architecture (3) Course feedback: 15%

## Note

- Please upload "PATTERN\_studentID.v" / "PATTERN\_p\_studentID.v" / "SP\_studentID.v" / "SP\_pipeline\_studentID.v" / "Report\_studentID.pdf" on New e3.
- Due Date: 23:59, Jan 6, 2025 (1st Demo)
- (If you have a late submission by 1 to 7 days, you will only get 80% of the score. We DO NOT accept any late submission after 7 days after the deadline.)
- If the uploaded file violates the naming rule, you will get 5 deduct points on this project.